

Roll No.

Total No. of Questions : 09]

[Total No. of Pages : 02

Paper ID [EC305]

(Please fill this Paper ID in OMR Sheet)

B.Tech. (Sem. - 5th)

LINEAR INTEGRATED CIRCUITS (EC - 305)

Time : 03 Hours

Maximum Marks : 60

Instruction to Candidates:

- 1) Section - A is **Compulsory**.
- 2) Attempt any **Four** questions from Section - B.
- 3) Attempt any **Two** questions from Section - C.

Section - A

Q1)

(10 × 2 = 20)

- a) What is another name for voltage to current converter?
- b) What is scaling amplifier?
- c) What type of voltage gain is provided by CE-CB configuration at higher frequencies?
- d) What is the affect on input resistance if three Op-amps are used as differential amplifier?
- e) What is effect of negative feedback in a non-inverting amplifier on input impedance and bandwidth?
- f) List one advantage of using compensated networks in Op-amps?
- g) How the input impedance of an ac voltage follower can be increased significantly?
- h) Define second order low pass filter? What does order of a filter signifies?
- i) Give any limitation of using Op-amp as a Comparator?
- j) Write an application of monostable multivibrator?

Section - B

(4 × 5 = 20)

- Q2) What is cascode amplifier? List its characteristics?
- Q3) Draw equivalent circuit of an Op-amp and discuss ideal voltage transfer curve?
- Q4) What is effect of variation in power supply voltages on offset voltage?
- Q5) Discuss voltage shunt feedback amplifier with a circuit diagram?
- Q6) Explain why open loop configurations are not used in linear applications?

Section - C

(2 × 10 = 20)

- Q7) Briefly explain the need for compensating networks in Op-amp circuits? Explain the difference between frequency response of internally compensated and non-compensated Op-amps?
- Q8) Discuss with circuit diagram operation of square and triangular wave generators?
- Q9) Describe PLL with block diagram. Also discuss applications of PLL in phase detector and voltage controlled oscillators?

