

B.Tech. (Sem. - 5th)
POWER ELECTRONICS
SUBJECT CODE : EE - 309
Paper ID : [A0417]

[Note : Please fill subject code and paper ID on OMR]

Time : 03 Hours

Maximum Marks : 60

Instruction to Candidates:

- 1) Section - A is **Compulsory**.
- 2) Attempt any **Four** questions from Section - B.
- 3) Attempt any **Two** questions from Section - C.

Section - A

Q1)

(10 x 2 = 20)

- a) What is PUT? Give its applications.
- b) Differentiate between holding and latching current in a thyristor.
- c) What is the role of dv/dt in the operation of a thyristor?
- d) What is a triac? Mention its applications.
- e) Mention drawbacks of series inverter.
- f) What is duty cycle of a chopper?
- g) What is a saturable reactor?
- h) Why is the output wave in a cycloconverter not sinusoidal?
- i) How can the output voltage of a cycloconverter be varied?
- j) What is the function of free wheeling diode?

Section - B

(4 x 5 = 20)

- Q2)** Explain the V-I Characteristics of Thyristors by elaborating the following:
- (a) latching current.
 - (b) holding current.
 - (c) on-state and off-state condition.
 - (d) turn-on and turn-off times.
 - (e) finger voltage.
- Q3)** Draw circuits and explain any two method of forced commutation of thyristors.
- Q4)** Explain the operation of a single phase half wave converter for R-load with neat circuit diagram and necessary waveforms.
- Q5)** Explain the operation of DC Morgan's Chopper for resistive load with neat circuit diagram and output voltage and current waveforms.
- Q6)** Draw and explain the simple SCR series inverter circuit employing class A type commutation. With the help of important waveforms. State the limitations of this inverter.

Section - C

(2 x 10 = 20)

- Q7)** (a) Explain the necessity of series and parallel connection of SCRs. Discuss the problems arising in series and parallel connections.
- (b) Explain the operation of three phase half-wave controlled converter with inductive load. Sketch the associated waveforms.
- Q8)** (a) What is the different pulse width modulation techniques used for inverters? Which of the schemes gives better quality of voltage and current?
- (b) A step-up chopper with a pulse width of $150 \mu\text{s}$ operating on 220 V, dc supply. Compute the load voltage if the blocking period of the device is $40 \mu\text{s}$.
- Q9)** Write short notes on any two of the following:
- (a) Single phase bridge cycloconverter.
 - (b) Speed control of DC motor drives.
 - (c) Jones chopper.

